


Name: _____

Parallel Circuits Worksheet

Show all work (including equations, substitutions and units) for full credit.

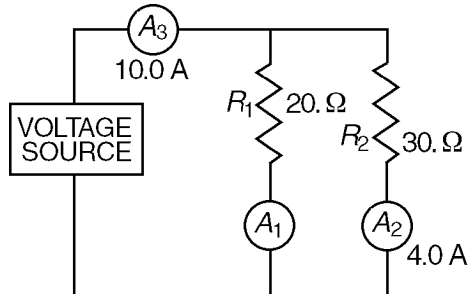Questions 1 and 2 refer to the following:


The diagram below shows two resistors and three ammeters connected to a voltage source.



- 1) What is the potential difference across the source in the circuit shown?

- 2) What is the current reading of ammeter A_1 in the circuit shown?

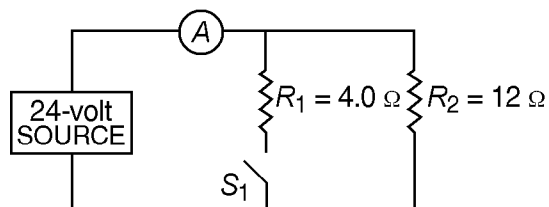
Questions 3 and 4 refer to the following:



- 3) If switch S_1 in the given diagram is open, the reading of ammeter A is

- 4) If switch S_1 in the given diagram is closed, the equivalent resistance of the circuit is

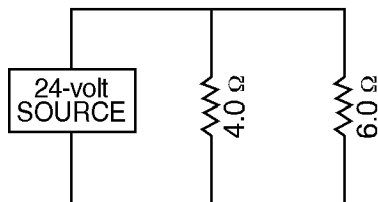- 5) The circuit diagram below shows two resistors connected to a 24-volt source of potential difference.




What is the total resistance of the circuit shown in the diagram?

- 6) An 18-ohm resistor and a 36-ohm resistor are connected in parallel with a 24-volt battery. A single ammeter is placed in the circuit to read its total current.


Draw a diagram of the circuit described using symbols from the *Circuit Symbols* physics reference table. [Assume the availability of any number of wires of negligible resistance.]

- 7) You are given a 12-volt battery, ammeter A , voltmeter V , resistor R_1 , and resistor R_2 . Resistor R_2 has a value of 3.0 ohms.
- (a) Using appropriate symbols from the *Circuit Symbols* physics reference table, draw and label a complete circuit showing:
- resistors R_1 and R_2 connected in parallel with the battery
 - the ammeter connected to measure the current through resistor R_1 , only
 - the voltmeter connected to measure the potential drop across resistor R_1
- (b) If the total current in the circuit is 6.0 amperes, determine the equivalent resistance of the circuit.
- (c) If the total current in the circuit is 6.0 amperes, determine the resistance of resistor R_1 . [Show all calculations, including the equation and substitution with units.]

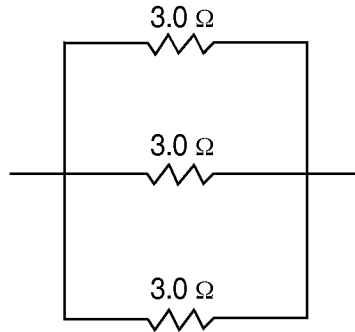- 8) What is the total resistance of the circuit segment shown in the diagram below?




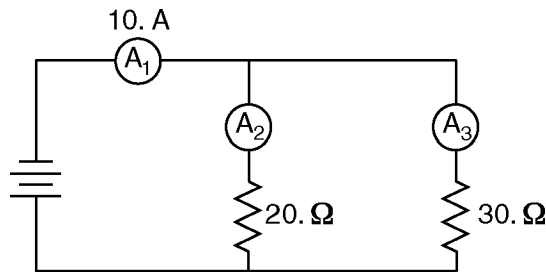- A) $27\ \Omega$ B) $1.0\ \Omega$ C) $3.0\ \Omega$ D) $9.0\ \Omega$
- 9) If a 15-ohm resistor is connected in parallel with a 30.-ohm resistor, what is the equivalent resistance?
- A) $10.\ \Omega$ B) $15\ \Omega$ C) $45\ \Omega$ D) $2.0\ \Omega$
- 10) In the circuit diagram shown below, ammeter A_1 reads 10. amperes.



What is the reading of ammeter A_2 ?




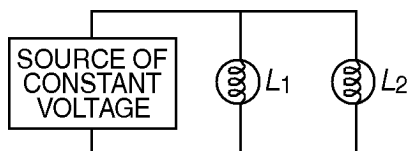
- A) 4.0 A B) 20. A C) 10. A D) 6.0 A
- 11) In the diagram below, lamps L_1 and L_2 are connected to a constant voltage power supply.




If lamp L_1 burns out, the brightness of L_2 will

- A) increase B) decrease C) remain the same

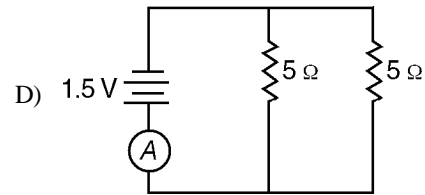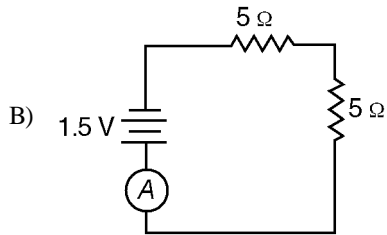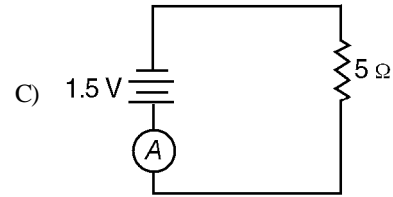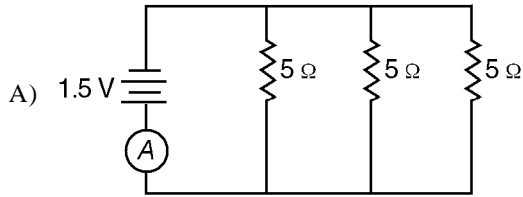12) In which circuit would ammeter A show the *greatest* current?



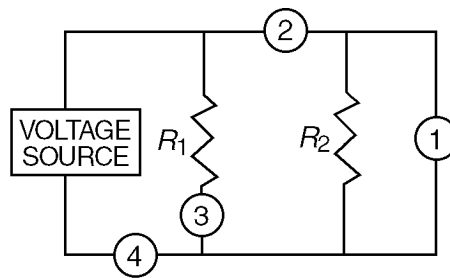13) Two resistors are connected to a source of voltage as shown in the diagram below.



At which position should an ammeter be placed to measure the current passing only through resistor R_1 ?

- A) 1 B) 2 C) 3 D) 4

14) Which circuit diagram below correctly shows the connection of ammeter A and voltmeter V to measure the current through and potential difference across resistor R ?

